


Circuits and Systems for Radio Frequency

Single Balanced Mixer Simulation

2025/2026

Single balanced mixer – Design example and testbench

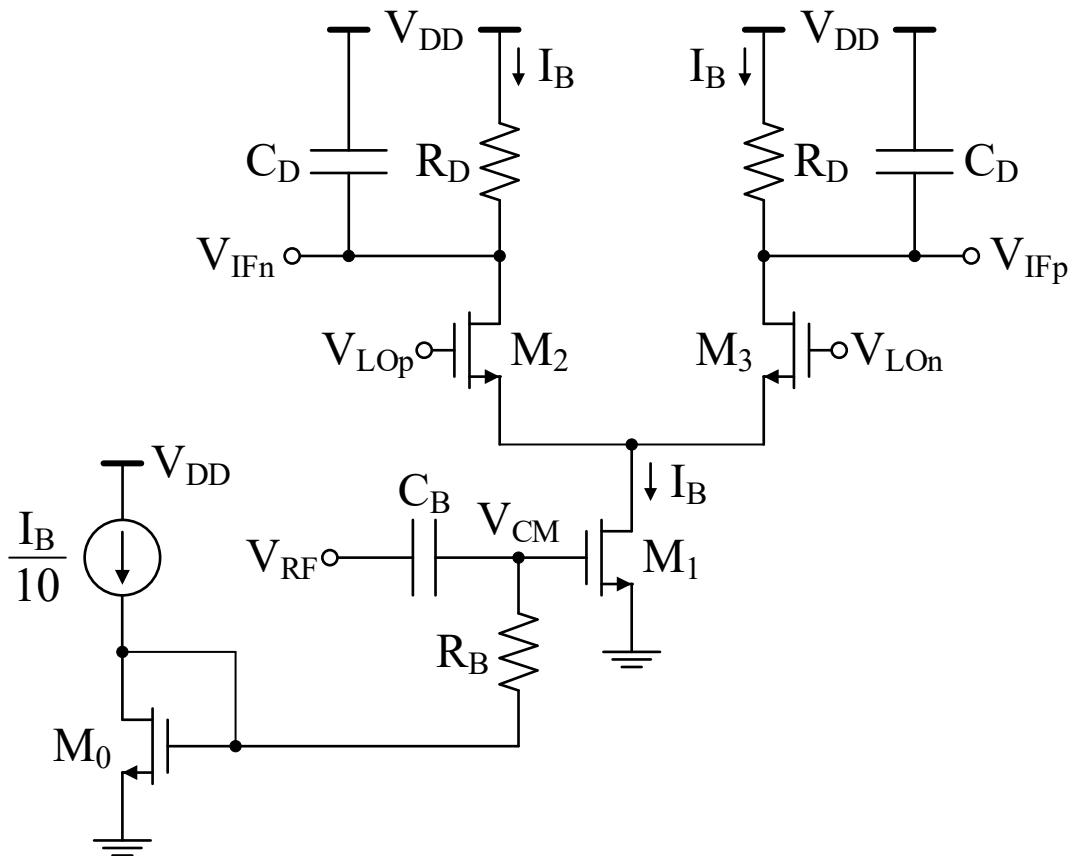- Only one branch is active at any given time
- Simulate circuit without and with capacitor C_D



Design:

- nch_lvt
- $V_{DD} = 1.2 \text{ V}$ and $V_{CM} = 0.475 \text{ V}$
- $W_F = \text{Width per finger}$ and $W_T = \text{Total width}$


	$W_F [\mu\text{m}]$	$W_T [\mu\text{m}]$	Fingers	$L [\mu\text{m}]$
M_0	0.44	3.52	8	0.06
M_1	3.88	31.04	8	0.06
$M_{2,3}$	2.10	4.20	2	0.06

$I_B [\text{mA}]$	$R_D [\text{k}\Omega]$	$R_B [\text{k}\Omega]$	$C_B [\text{pF}]$	$C_D [\text{pF}]$
1.0	0.5	10.0	1.0	50.0

$f_{RF} [\text{MHz}]$	$f_{LO} [\text{MHz}]$	$V_{amp} [\text{dBm}]$
90.0~99.0	100.0	-30


Procedure for PSS only simulations:

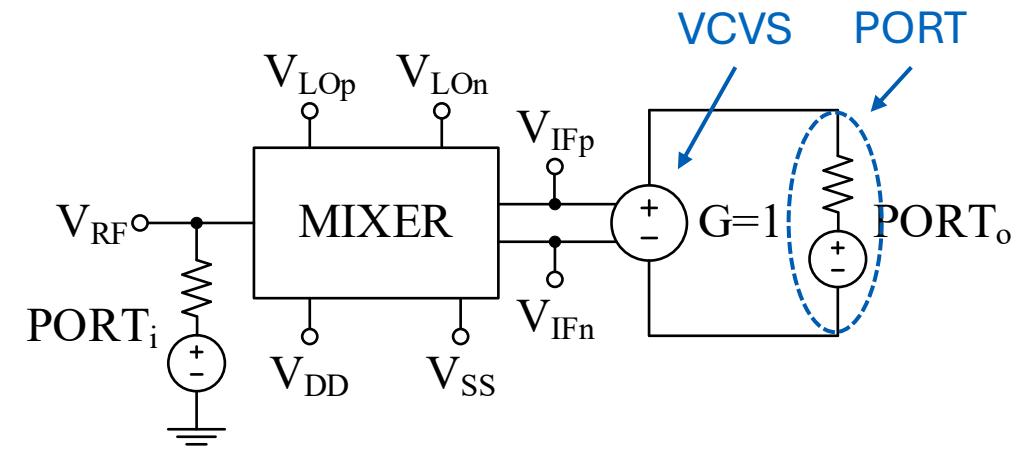- Input port (PORT_i) – Simulate circuit for different port resistances (50 and 1000 Ω)
 - Define port as a sine signal with a given frequency and amplitude
 - Output port (PORT_o) with 100 Ω
-
- **PSS simulation:**
 - Beat frequency = $f_{\text{LO}} - f_{\text{RF}}$
 - Number of harmonics = 100







Single balanced mixer – Flat schematic example

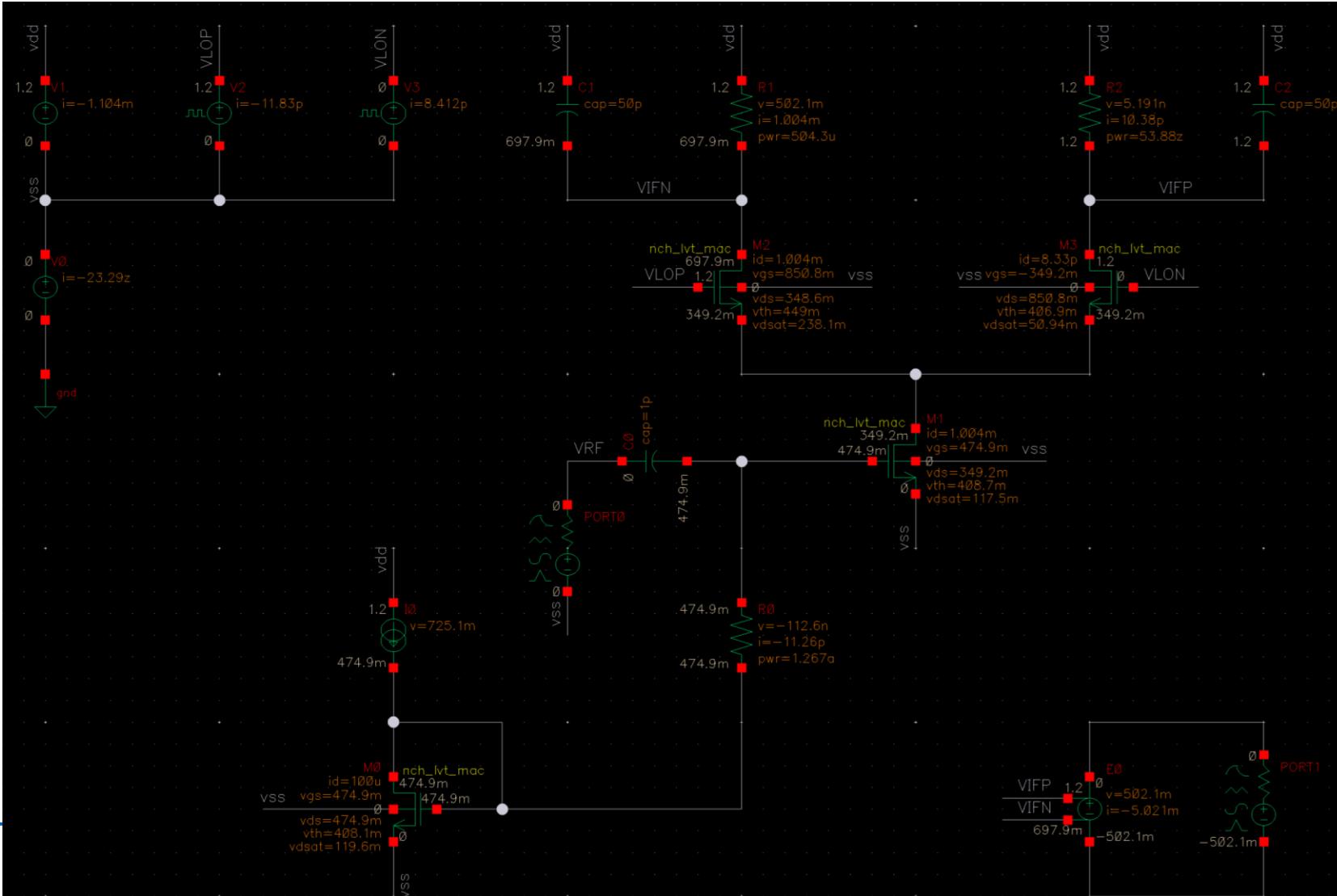- Check PFR to make sure design is correct



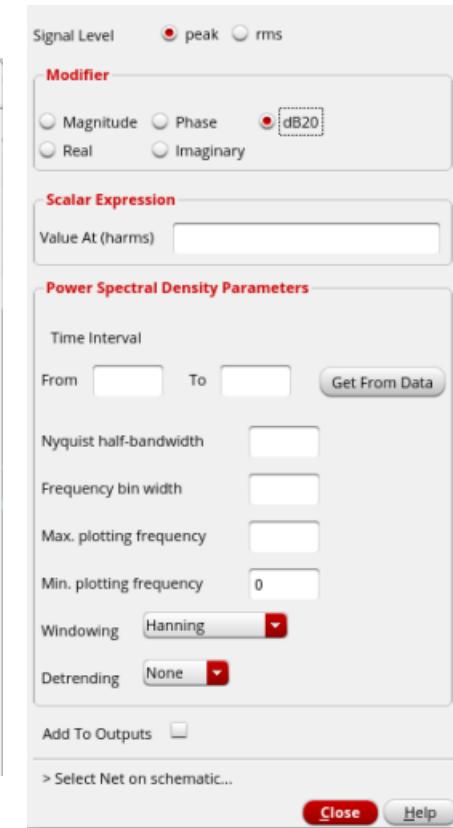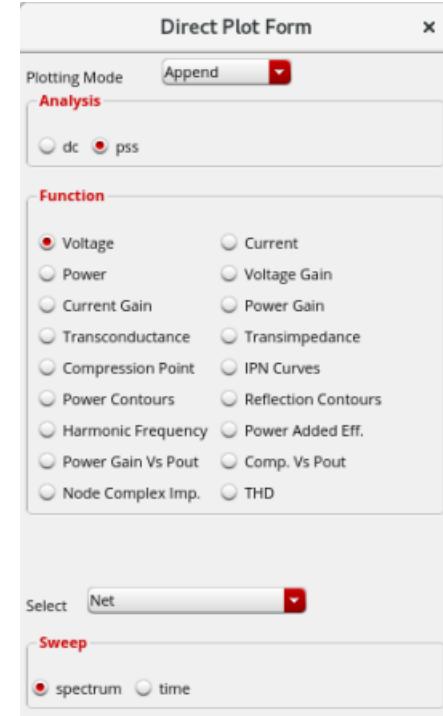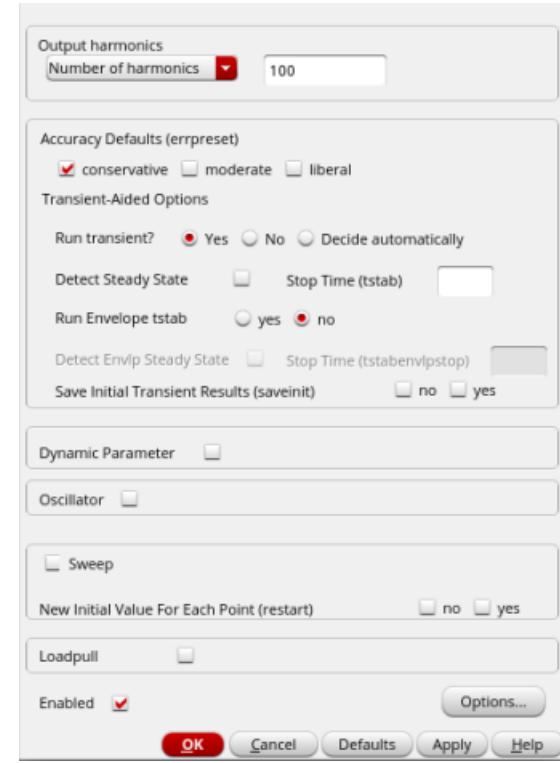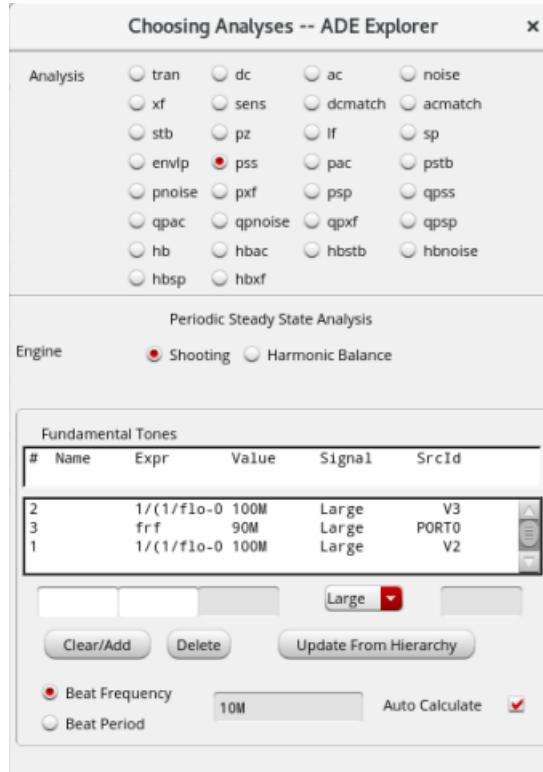
Simulation window/result plotting for PSS only simulation




PSS simulation configurations

Direct plot configurations

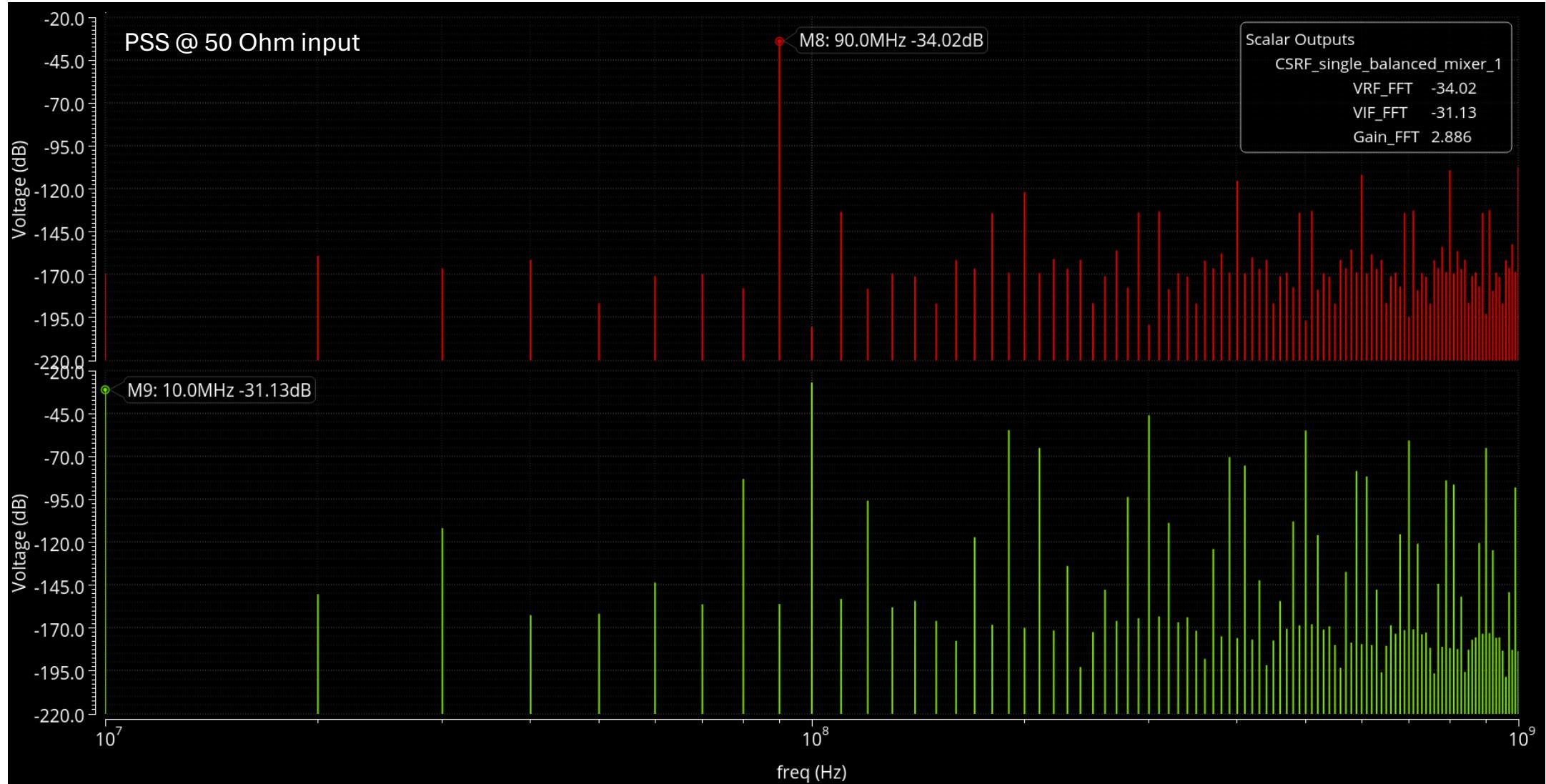Single balanced mixer – Simulation results (PSS)




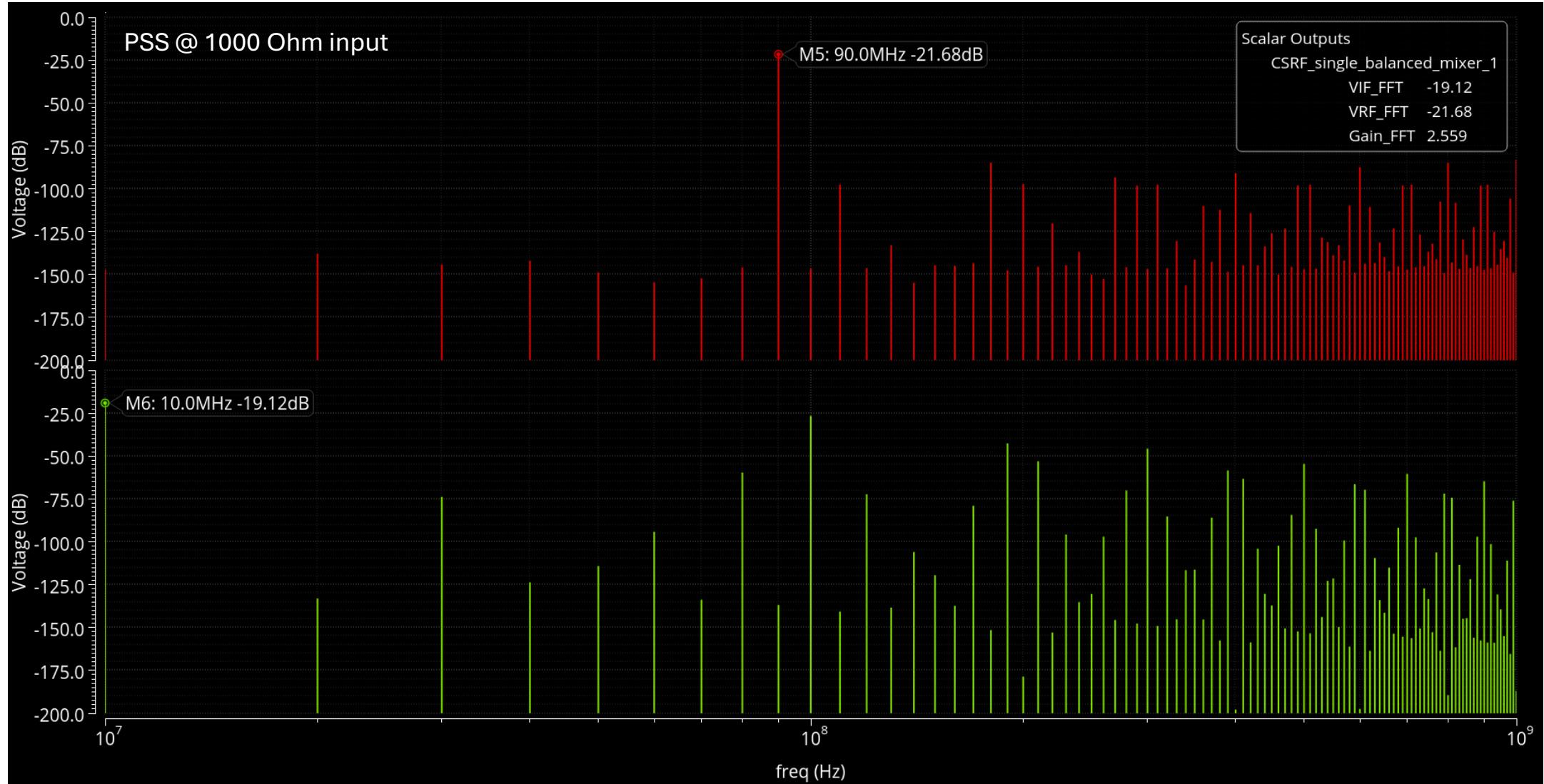Single balanced mixer – Simulation results (PSS)







Procedure for PSS+(PAC/PNOISE) simulations:

- Input port (PORT_i) – Simulate circuit for different port resistances (50 and 1000 Ω) and PAC magnitude = 1
 - For frequency simulations input port must be configured to a DC source
- Output port (PORT_o) with 100 Ω
- **PSS simulation:**
 - Beat frequency = f_{LO}
 - Number of harmonics = 100
- **PAC simulation for conversion gain simulation:**
 - Start Frequency = f_{LO}
 - Stop Frequency = $2 \times f_{\text{LO}}$
 - Maximum sidebands = 1
 - Use a high number of points (>1000)
 - To plot, select “Voltage Gain”, and the “sideband” sweep option with output sideband = -1 and input = 0

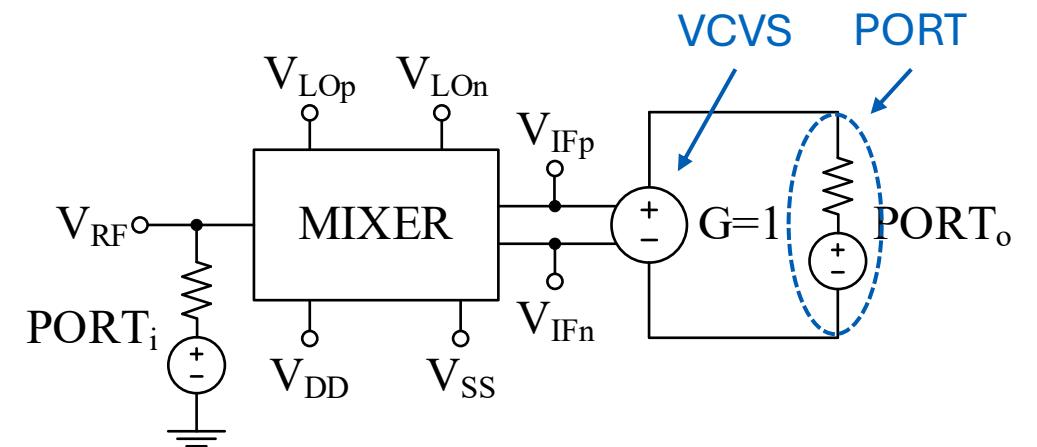

Important note: The voltage gain option is necessary because, even with PAC magnitude = 1, the input magnitude is dependent on the circuits input impedance

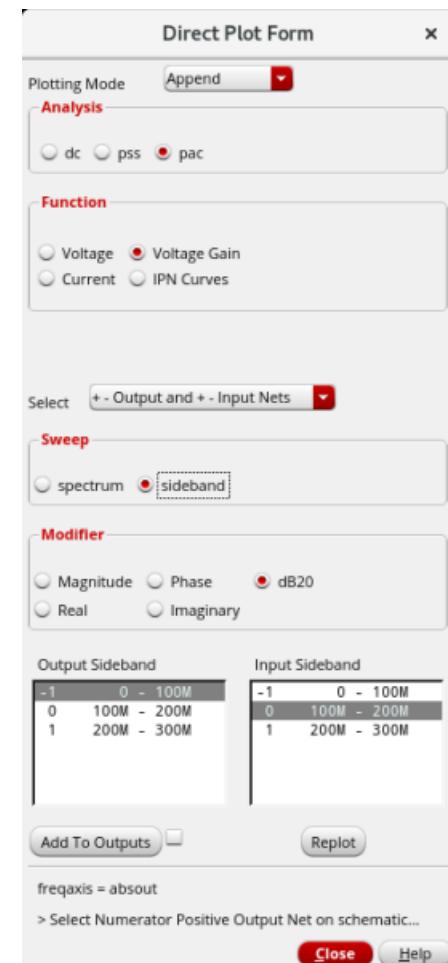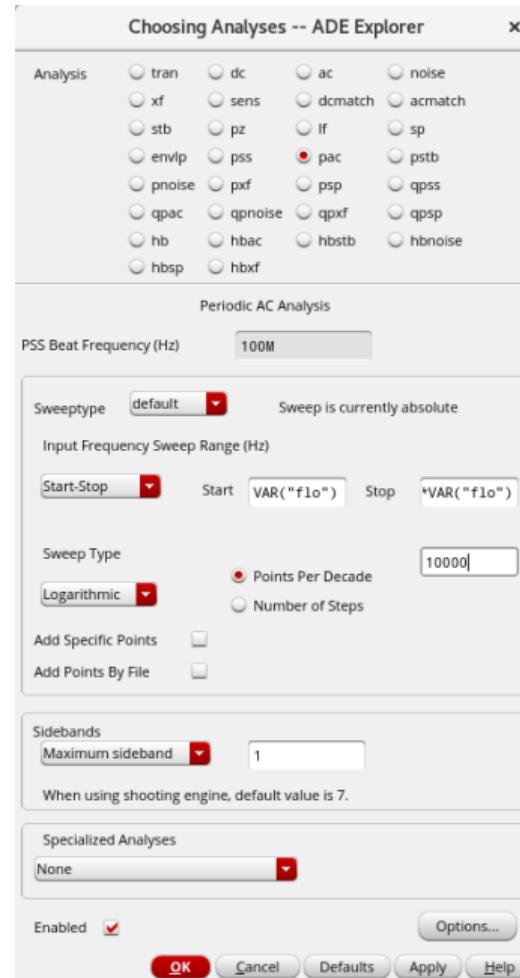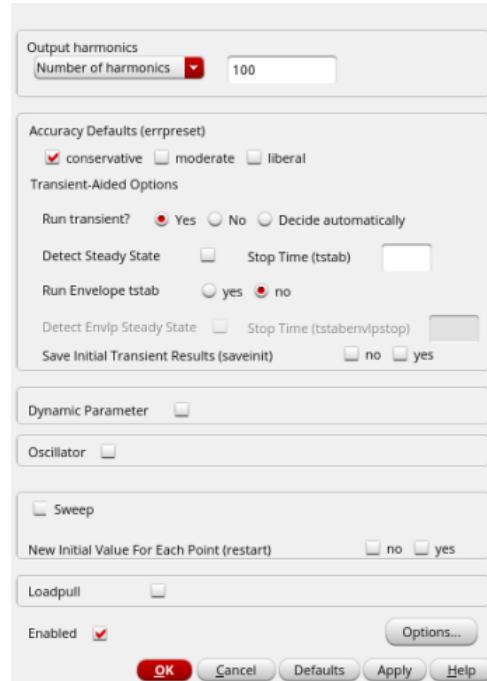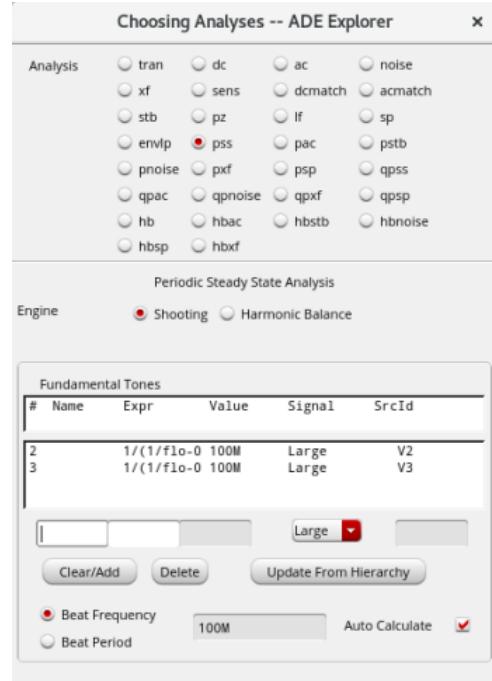
Simulation window/result plotting for PSS+PAC simulation



PSS+PAC simulation configurations


Direct plot configurations

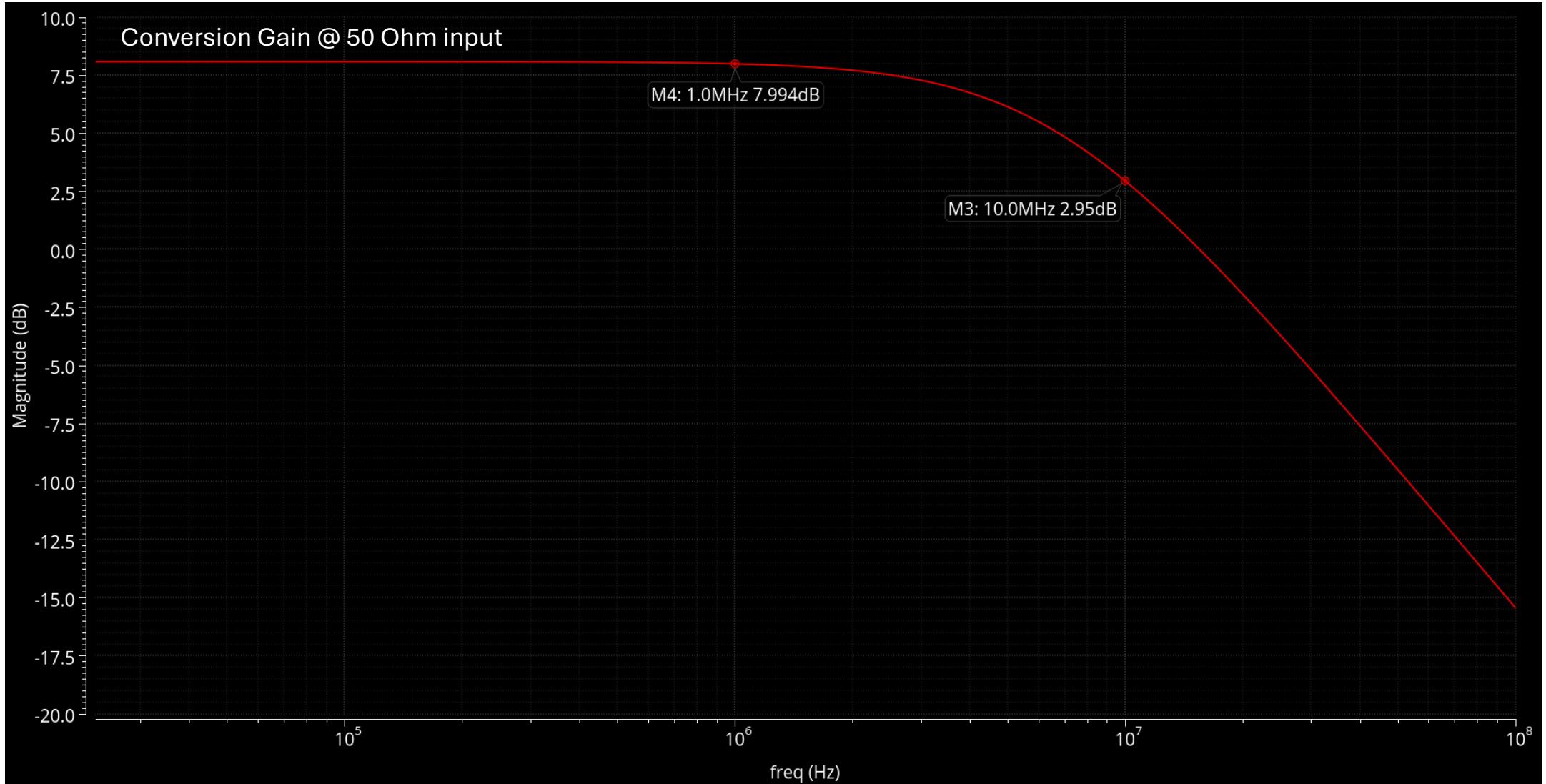Single balanced mixer – Simulation results (PSS+PAC)




Single balanced mixer – Simulation results

(obtained from a transient simulation)



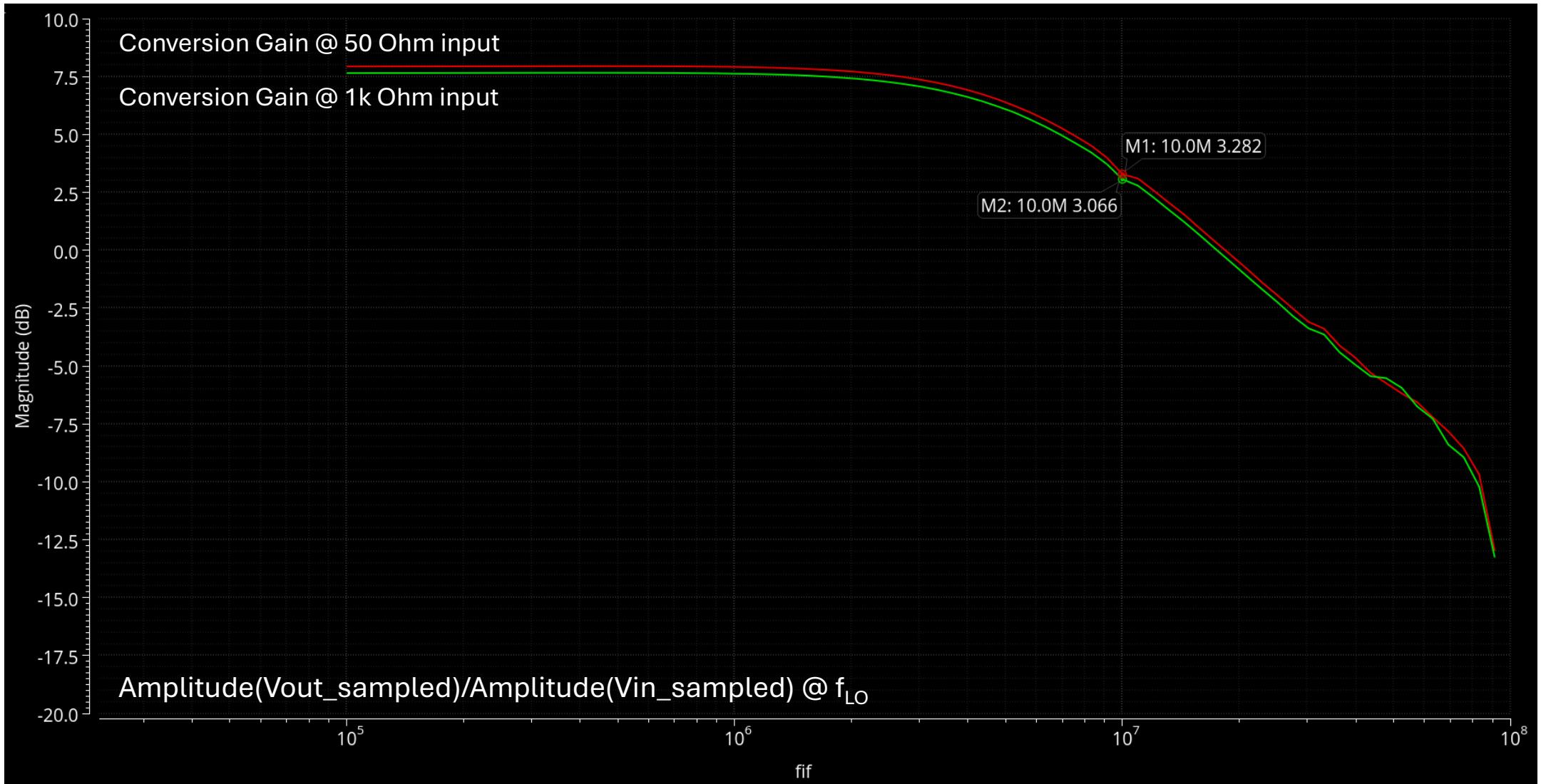


Procedure for PSS+(PAC/PNOISE) simulations:

- Input port (PORT_i) – Simulate circuit for different port resistances (50 and 1000 Ω) and PAC magnitude = 1
 - For frequency simulations input port must be configured to a DC source
- Output port (PORT_o) with 100 Ω
- **PSS simulation:**
 - Beat frequency = f_{LO}
 - Number of harmonics = 100
- **PNOISE simulation for noise figure simulation:**
 - Start Frequency = 1
 - Stop Frequency = f_{LO}
 - Maximum sidebands = 10
 - Reference sideband = -1
 - Select output and input ports

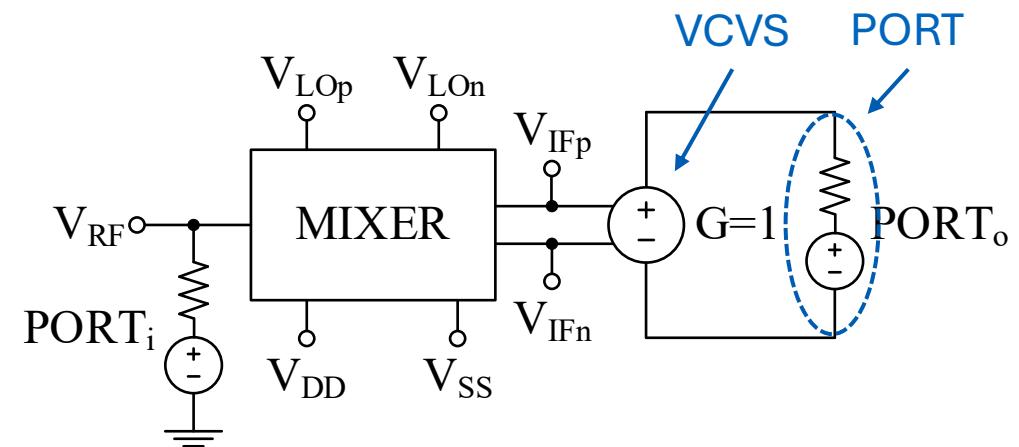

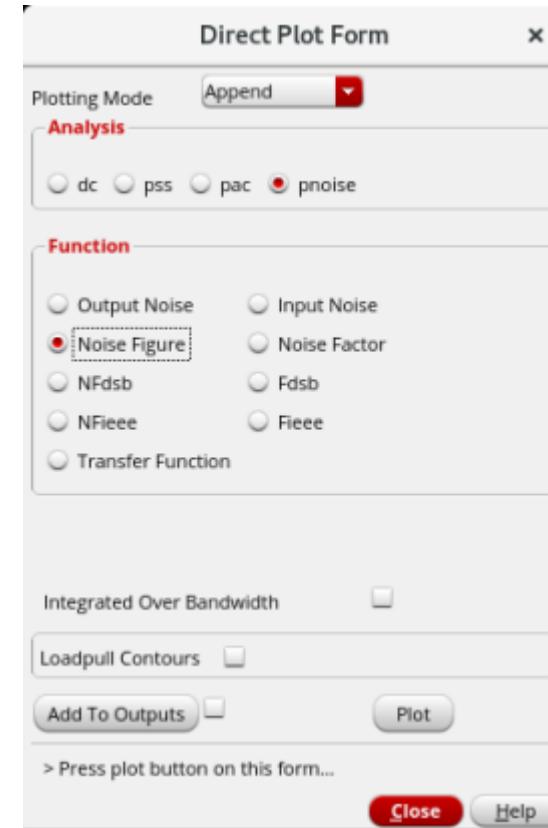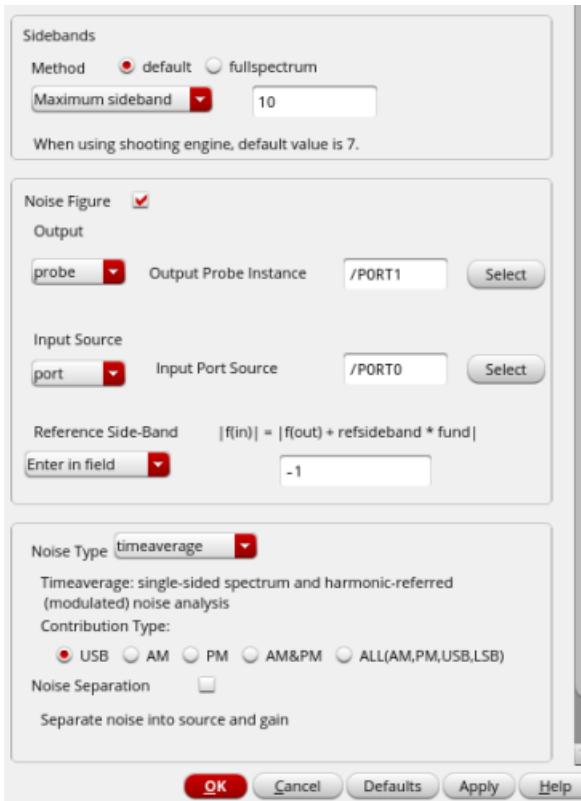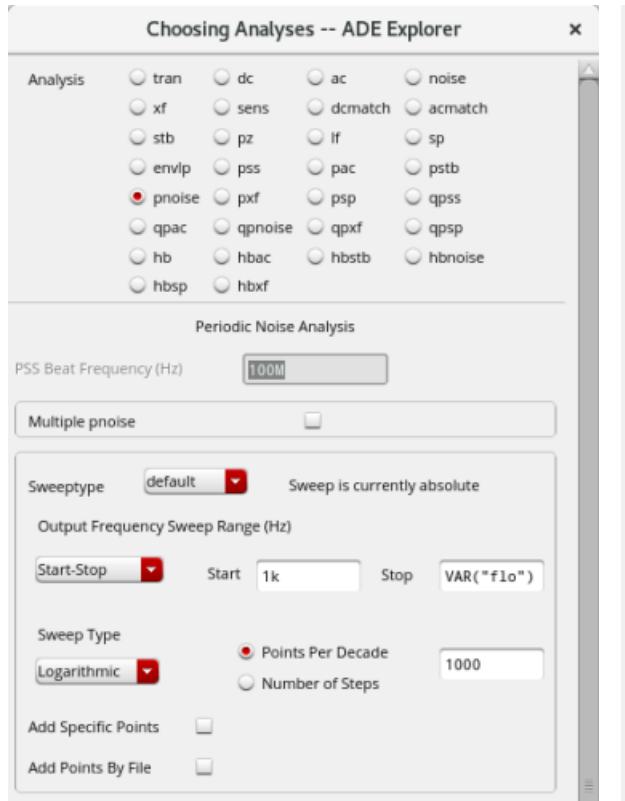
Simulation window/result plotting for PSS+PNOISE simulation



PNOISE simulation configuration
(see slide 9 for PSS simulation configuration)


Direct plot configurations

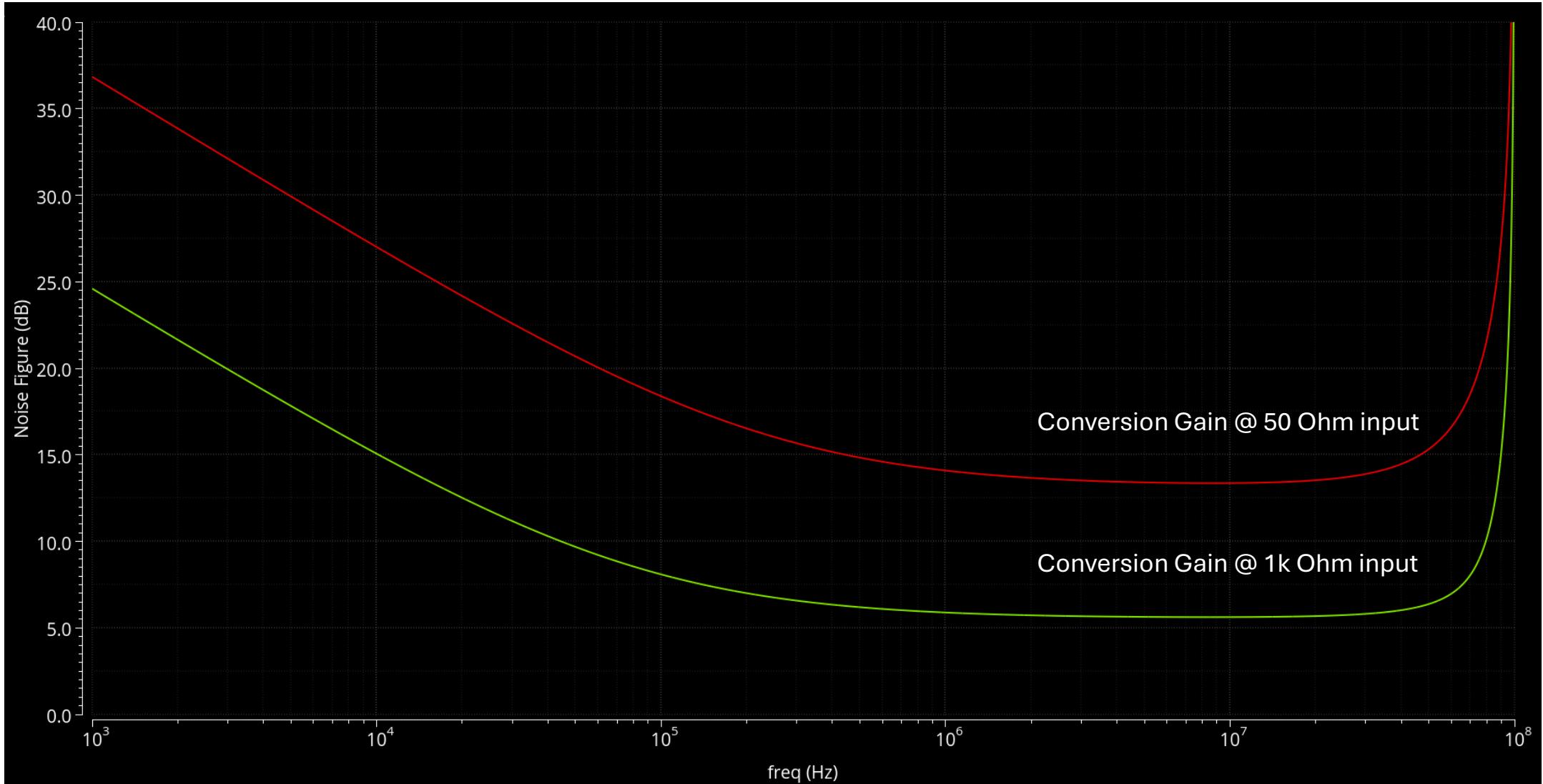Single balanced mixer – Simulation results (PSS+PNOISE)





Procedure for 1dB compression point simulation using PSS:



- Input port (PORT_i) – Simulate circuit for different port resistances (50 and 1000 Ω)
 - Define port as a sine signal with a given frequency and amplitude
- Output port (PORT_o) with 100 Ω
- **PSS simulation:**
 - Beat frequency = $f_{\text{LO}} - f_{\text{RF}}$
 - Number of harmonics = 100
 - Activate the sweep box
 - Define design variable that controls input amplitude
 - Define sweep range from -60 to 0 and define step
 - To plot select “Compression Point”, an “Input Power Extrapolation Point” inside the linear region and the f_{IF} frequency in the “1st Order Harmonic” table

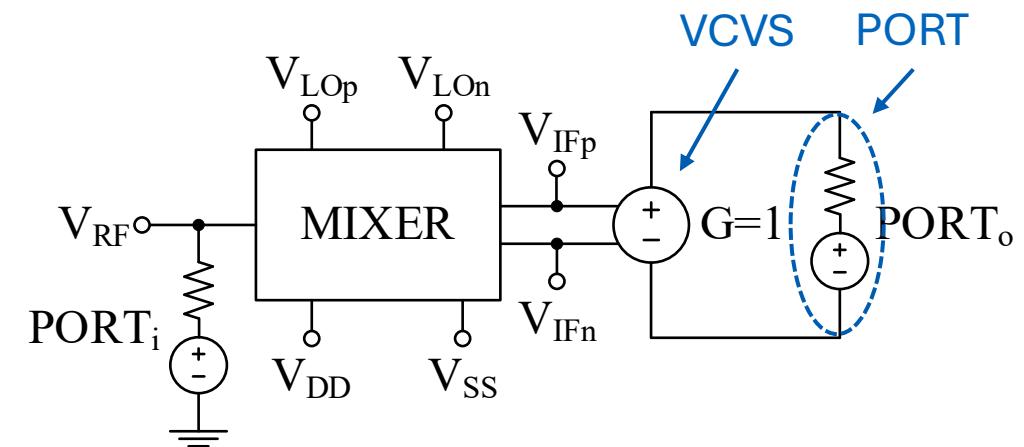

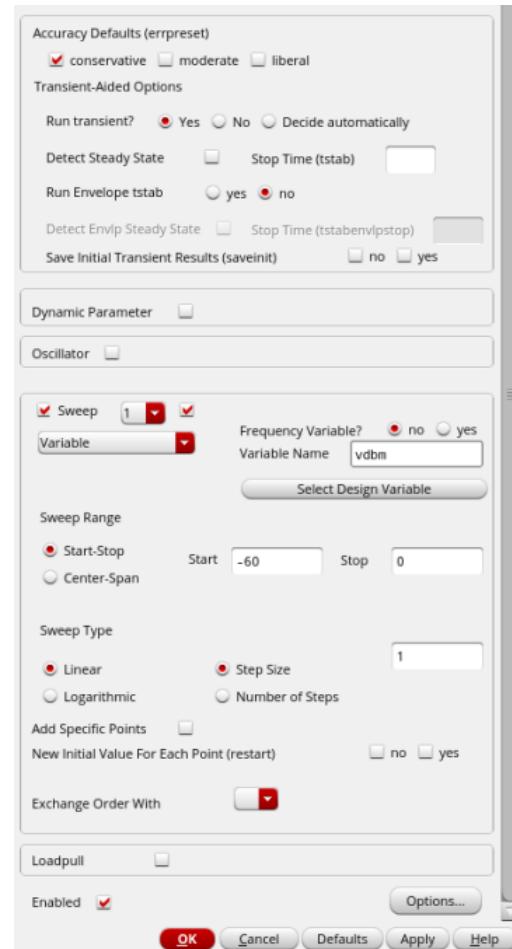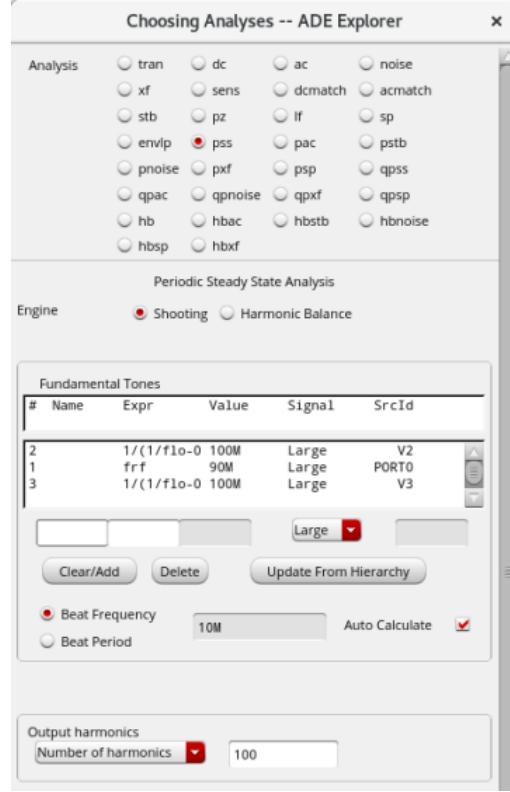Simulation window/result plotting for PSS only simulation




PSS simulation configuration for 1dB CP

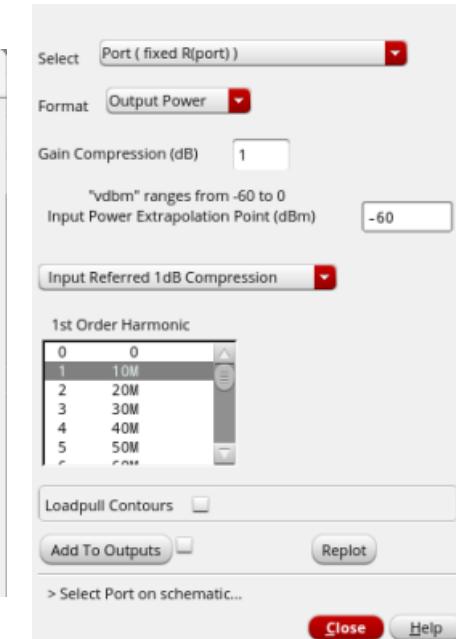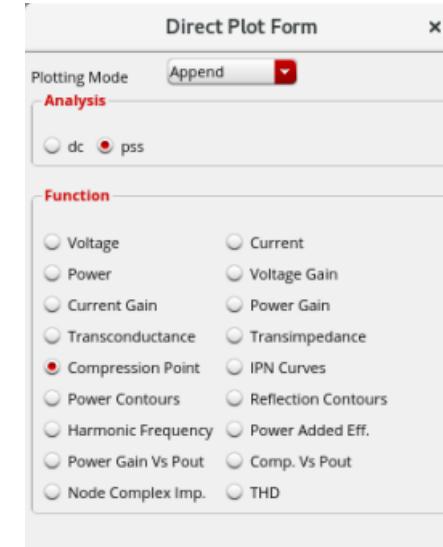


Direct plot configurations

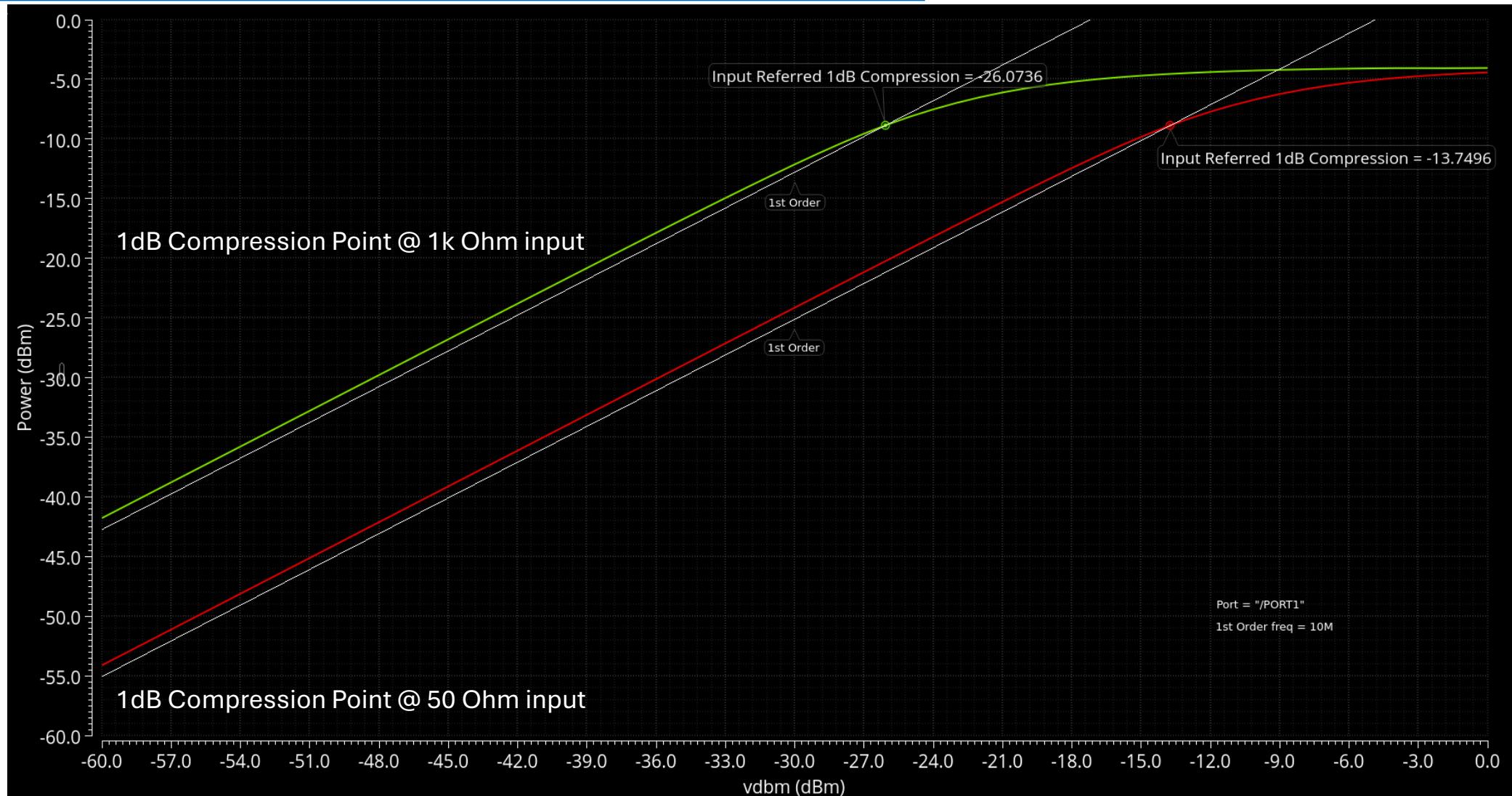Single balanced mixer – Simulation results (PSS)




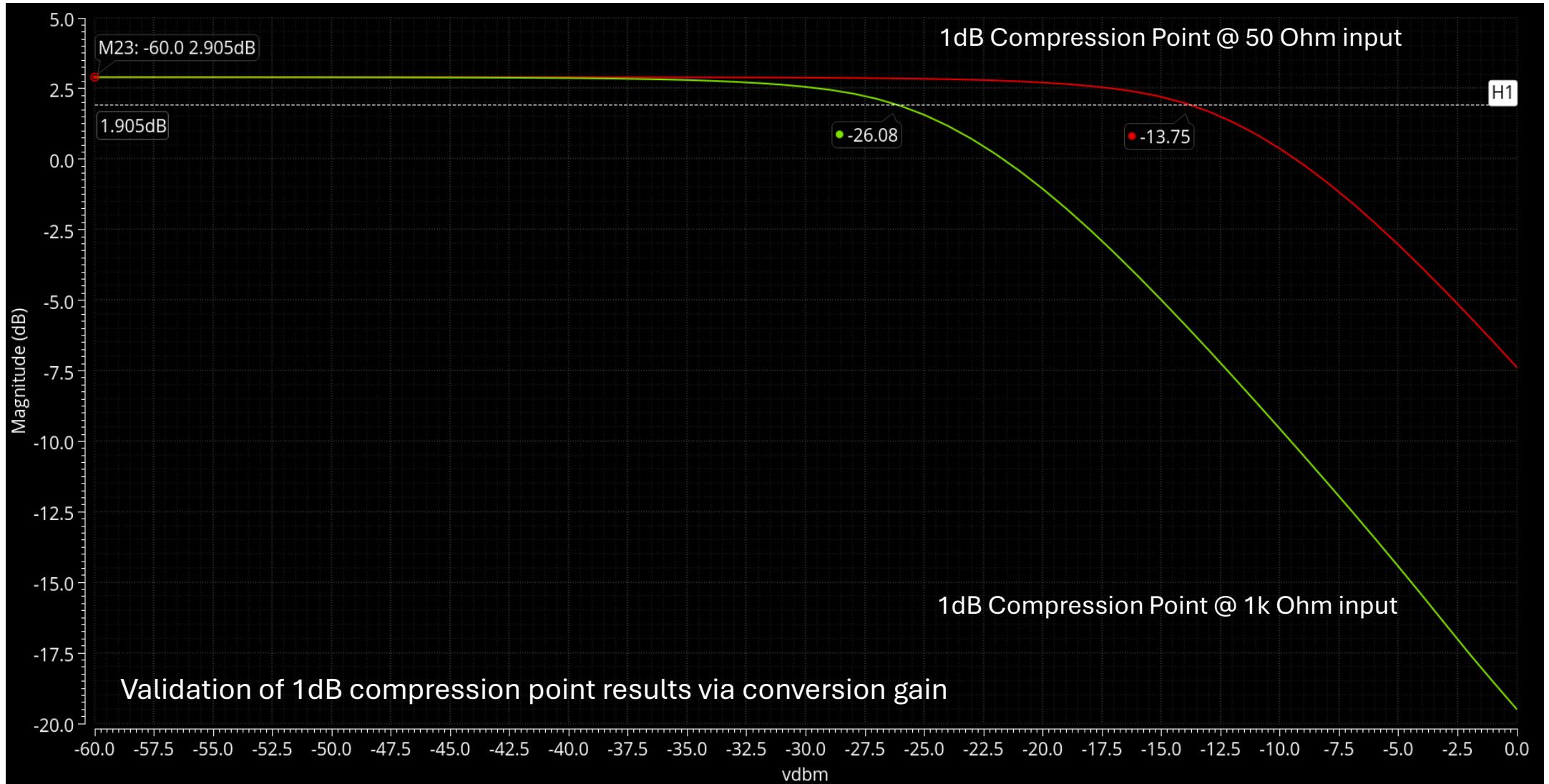Single balanced mixer – Simulation results (PSS)







Procedure for IIP3 simulation using PSS:

- Input port (PORT_i) – Simulate circuit for different port resistances (50 and 1000 Ω)
 - Define port as a sine signal with two tones (f_{RF} and $f_{\text{RF}2}$) and same amplitude
- Output port (PORT_o) with 100 Ω
- **PSS simulation:**
 - Beat frequency = $f_{\text{RF}2} - f_{\text{RF}}$
 - Number of harmonics = 100
 - Activate the sweep box and
 - Define design variable that controls input amplitude
 - Define sweep range from -60 to 0 and define step
 - To plot select “IPN Curves”, choose “Variable Sweep” in “Circuit Input Power” and an “Input Power Extrapolation Point” inside the linear region. In the “1st Order Harmonic”, choose f_{IF} (considering there is no second tone). In the “3rd Order Harmonic”, choose f_{IFx} or f_{IFy} (see below), whichever is closer to f_{IF}
- **Frequency examples:**
 - $f_{\text{RF}} = 90 \text{ MHz}$ and $f_{\text{RF}2} = 91 \text{ MHz}$
 - Calculate $f_x = 2 \times f_{\text{RF}} - f_{\text{RF}2} = 89 \text{ MHz}$ and $f_y = 2 \times f_{\text{RF}2} - f_{\text{RF}} = 92 \text{ MHz}$
 - Perform down-conversion: $f_{\text{IFx}} = f_x - f_{\text{LO}} = 11 \text{ MHz}$ and $f_{\text{IFy}} = f_y - f_{\text{LO}} = 8 \text{ MHz}$

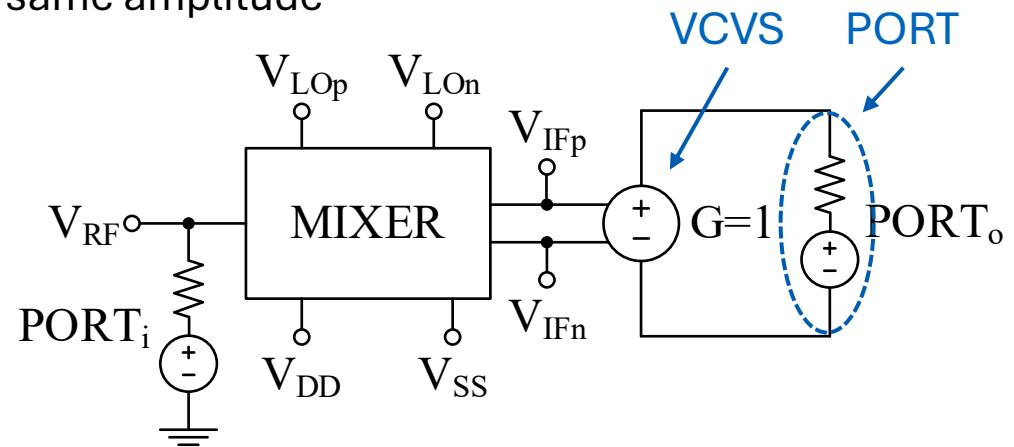

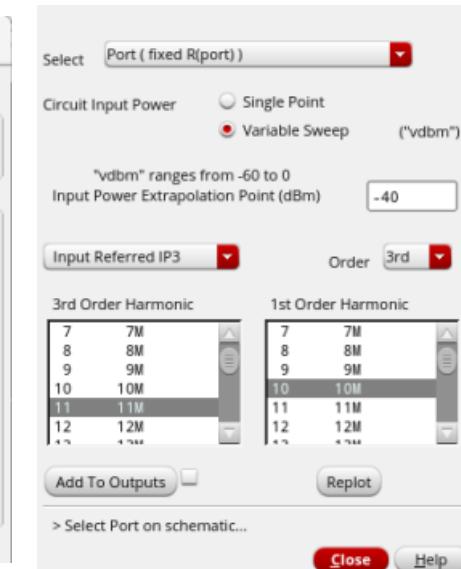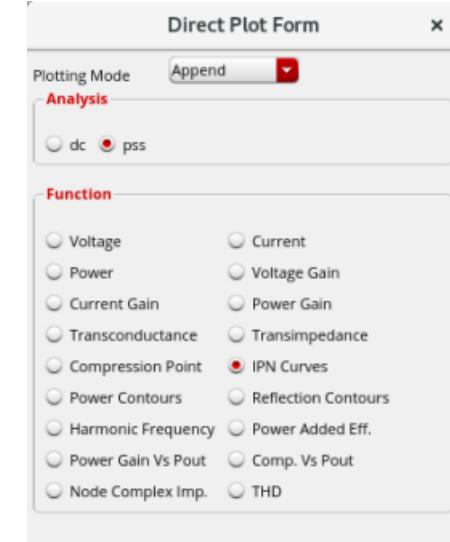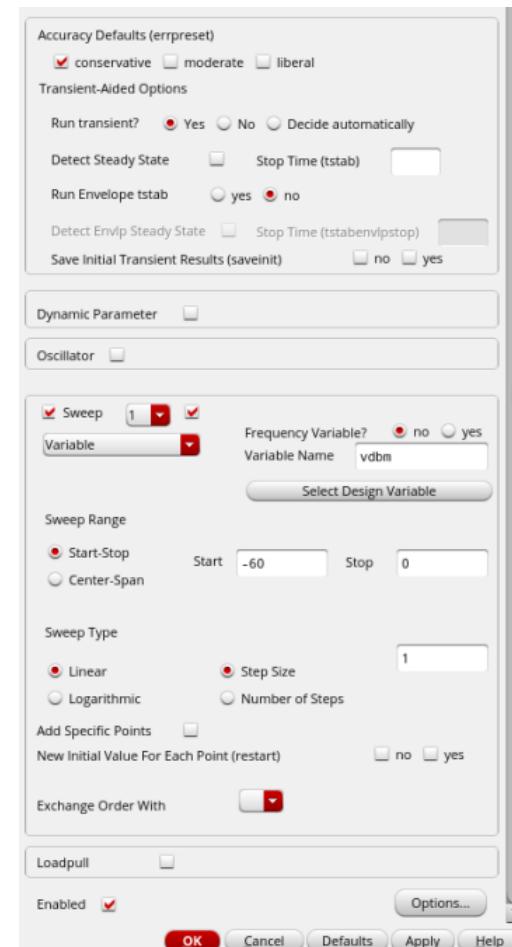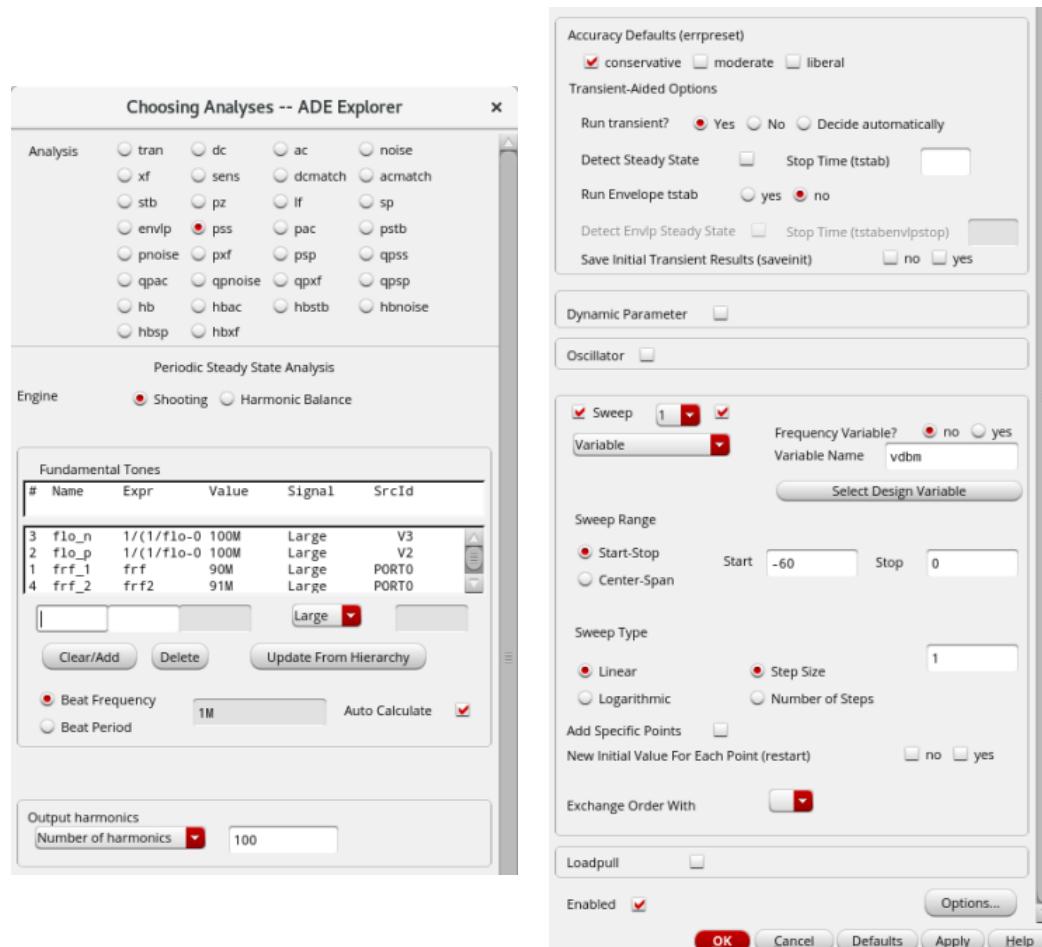
Simulation window/result plotting for PSS only simulation



PSS simulation configuration for IIP3

Direct plot configurations

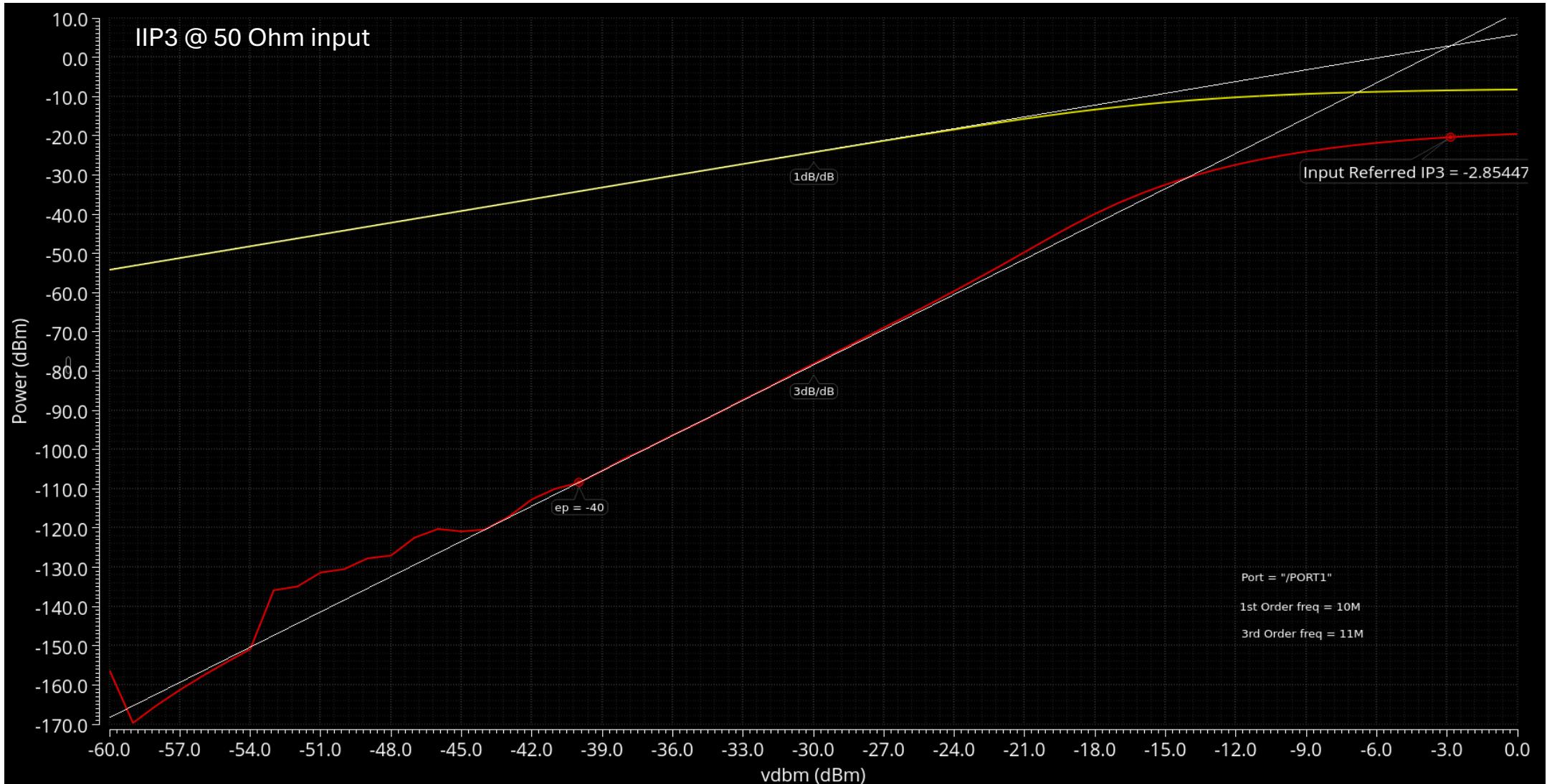Single balanced mixer – Simulation results (PSS)



Single balanced mixer – Simulation results (PSS)

